

ECE 559

Shiyu Li, Zhiyao Xie

Contents

- Function Overview
- Top-Level Schematic
- Sub-Module Design & Functional Simulation
 - CRC24
 - Control Path
 - Block Size Computation
- Timing & Resource Analysis
- Subsystem Functional Simulation

Function Overview

- Simplifications:
 - Maximum Transfer Block Size is 1530Bytes = 12240Bits
 - CRC is attached only if the segmentation is performed, i.e., more than one code block is required.
 - Two possible block size: *(Might be different with project spec. but we followed the 3GPP Document and are proved by prof.)*
 - ≤ 1056 bits
 - 1 small block, no CRC
 - > 1056 bits and ≤ 6144 bits
 - 1 big block, no CRC
 - > 6144 bits and $\leq (6144 + 1056 - 24 \cdot 2) = 7152$ bits
 - [small block w/filling, big block] all with CRC
 - > 7152 bits and $\leq 12,240$ bits
 - [big block w/filling, big block] all with CRC


Function Overview

- Input interface assumption:
 - The size of the transfer block is asserted a cycle ahead of the data
 - The transmission of the data is performed with the same clock, same speed.
 - There's no lag, no corruption.
 - Input data FIFO will not be full.
 - We don't need to wait for the transfer block data during the process.


Function Overview

- Desired output timing:
 - **Start** Signal Asserted
 - Next Cycle, **block_size** signal asserted, 0 for small block, 1 for large block
 - The same cycle, the first bit of the data begin to transfer.
 - If current bit is the filling bit, the **filling** signal will be asserted **at the same cycle**.
 - If current bit is the CRC bit, the **crc** signal will be asserted **at the same cycle**.
Note: Filling bits also participate the computation of CRC as 0.
 - **Stop** signal will be asserted the next cycle of the last bit of the data block(including CRC).
- *Orange Part can be easily changed per request.

Top-Level Schematic

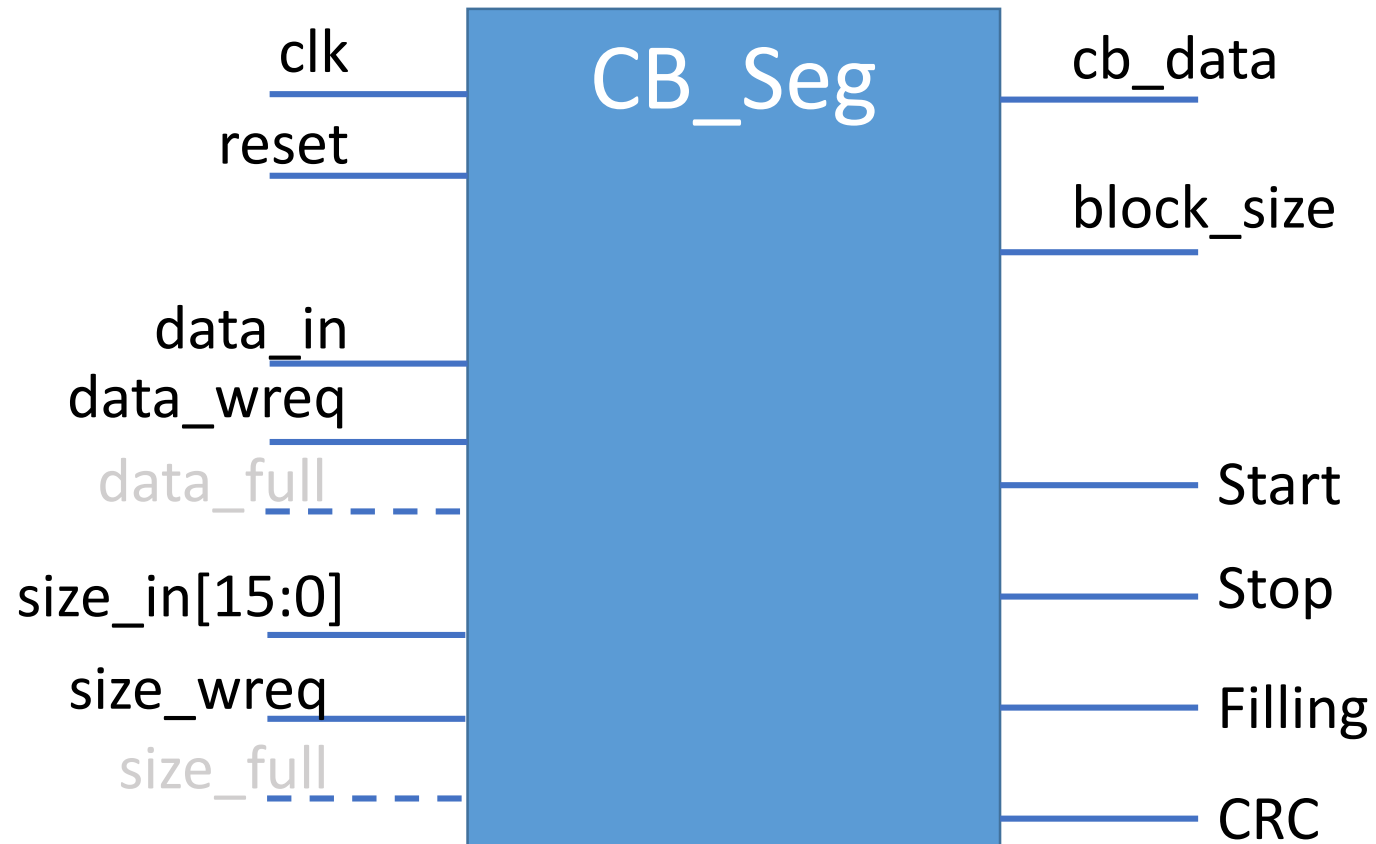

Top-Level Schematic

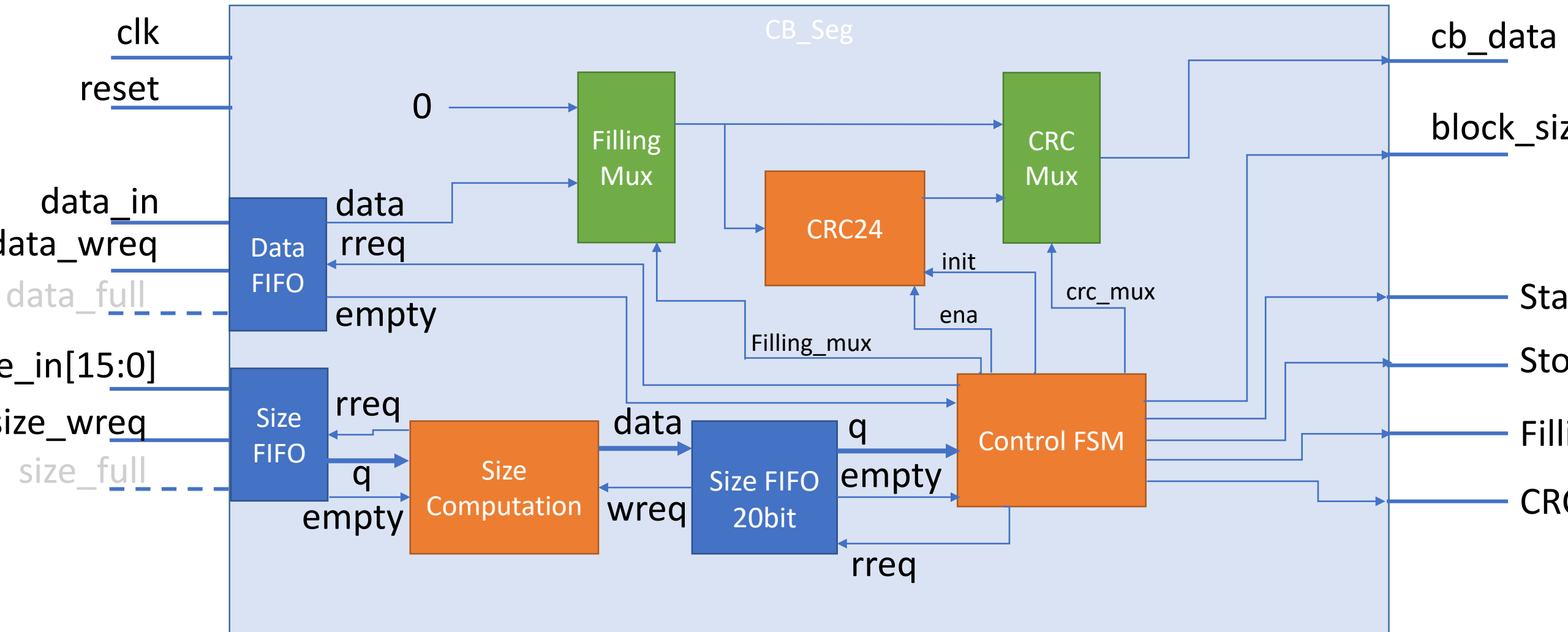

Sub-Module Design & Functional Simulation

- CRC24
- Control Path
- Block Size Computation


CRC24 Implementation

- $g_{\text{CRC24A}}(D) = [D^{24} + D^{23} + D^{18} + D^{17} + D^{14} + D^{11} + D^{10} + D^7 + D^6 + D^5 + D^4 + D^3 + D + 1]$ and;
 - $g_{\text{CRC24B}}(D) = [D^{24} + D^{23} + D^6 + D^5 + D + 1]$ for a CRC length $L = 24$ and;
 - $g_{\text{CRC16}}(D) = [D^{16} + D^{12} + D^5 + 1]$ for a CRC length $L = 16$.
 - $g_{\text{CRC8}}(D) = [D^8 + D^7 + D^4 + D^3 + D + 1]$ for a CRC length of $L = 8$.
-
- Various GF for different kinds of block.
 - For LTE Data Blocks, we use CRC24B.
 - Modified based on the LFSR implementation of Homework2

CRC24 Sanity Check

Input Sequence: 0101010101010100000111110101010101010101

Desired Output: 011111011110100111100000

 


After de-assert shift function, we'll get the shifted output.

Compute Desire Result with: <https://leventozturk.com/engineering/crc/>

Control Path

- Port:
 - With Size FIFO:
 - Empty, Read Request, [19:0]Data
 - With Mux
 - Filling sel, Crc sel
 - With Data FIFO:
 - Empty, Read Request, Data
 - With CRC24:
 - Init, Compute_ena, nshift
 - Control Signals Output
 - Start, Stop, Filling, CRC

FSM Plot

 


- Follow the Encoding Scheme in Quartus' doc
- Fault-tolerant One-hot coding

```


//FSM State Encoding
//Following the Quartus Encoding Scheme
parameter IDLE      = 8'b00000000,
           READ_REQ  = 8'b00000011,
           READ_SIZE = 8'b00000101,
           LOAD_SIZE = 8'b00001001,
           FILLING    = 8'b00010001,
           READ_DATA  = 8'b00100001,
           OUT_CRC    = 8'b01000001,
           NEXT_BLOCK = 8'b10000001;
    
```

FSM Behavior

 

- **IDLE**
 - Initialize CRC register & crc_req register **[Moore]**
- **READ_REQ**
 - Assert rreq signal of the size FIFO **[Moore]**
- **READ_SIZE**
 - Load C+, C- into 2-bits register, Filling Bits to the counter. **[Moore]**
 - Based on C+ and C-, write crc_req register. **[Mealy]**


FSM Behavior

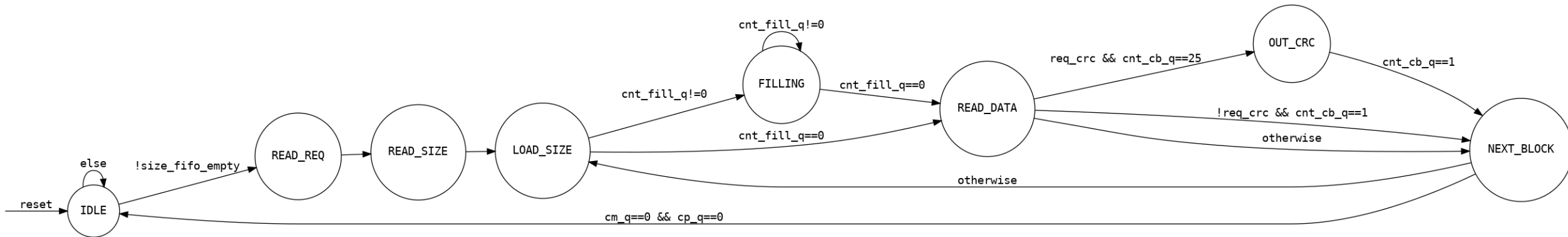

- **LOAD_SIZE**

- Read C+ and C- register, decide the next code block to send. Small block first.
- Load the next block size into the cb counter. **[Mealy]**
- De-assert crc compute enable **[Moore]**
- Update C+ and C- register. **[Mealy]**
- Based on filling or not, pre-assert the rreq of data fifo **[Mealy]** and enable the cb counter. **[Moore]**
- Assert Start signal. **[Moore]**


FSM Behavior

 

- **FILLING**


- Assert filling_mux signal. **[Moore]**
- Assert CRC_enable. **[Moore]**
- Assert enable of the filling counter if it's not the last bit of filling. **[Mealy]** *(To avoid underflow of the counter since we use the value of the counter later)*
- Pre-assert rreq if it's the last bit of filling. **[Mealy]**

FSM Behavior

 

- **READ_DATA**
 - Assert filling_mux, CRC_enable, counter enable **[Moore]**
 - Assert rreq if it's not the last bit of the data. **[Mealy]**
- **OUT_CRC**
 - Let CRC register running in shift register mode.
 - Assert counter enable, crc_mux **[Moore]**
 - De-assert rreq, nshift_crc **[Moore]**

FSM Behavior

 


- **NEXT_BLOCK**
 - Initialize CRC register. **[Moore]**
 - Assert Stop Signal. **[Moore]**
 - Keep Assert CRC if required. **[Mealy]**


Functional Simulation

- Reduce Block size to 32 (small block) and 48(big block) for sanity check.
- Input Covers all the four situations mentioned above.

Functional Simulation

 


Functional Simulation

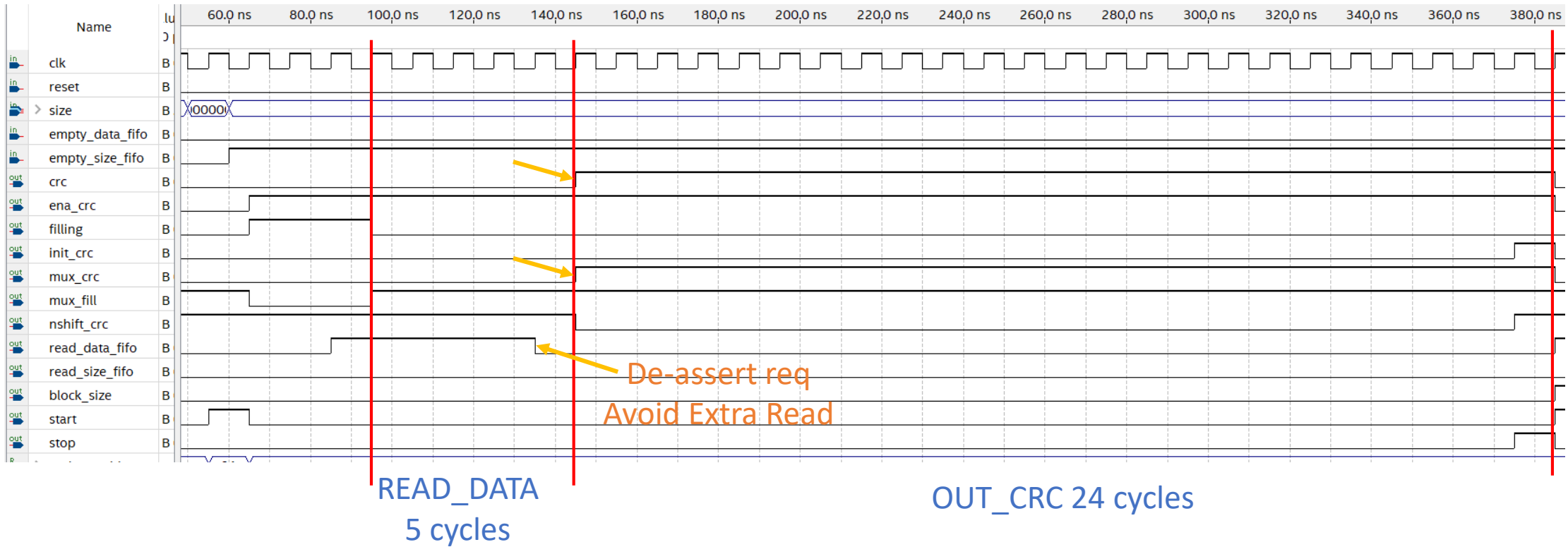


- 1 big block & 1 small block
- 3 filler bits


Functional Simulation

 

Functional Simulation

 

Functional Simulation

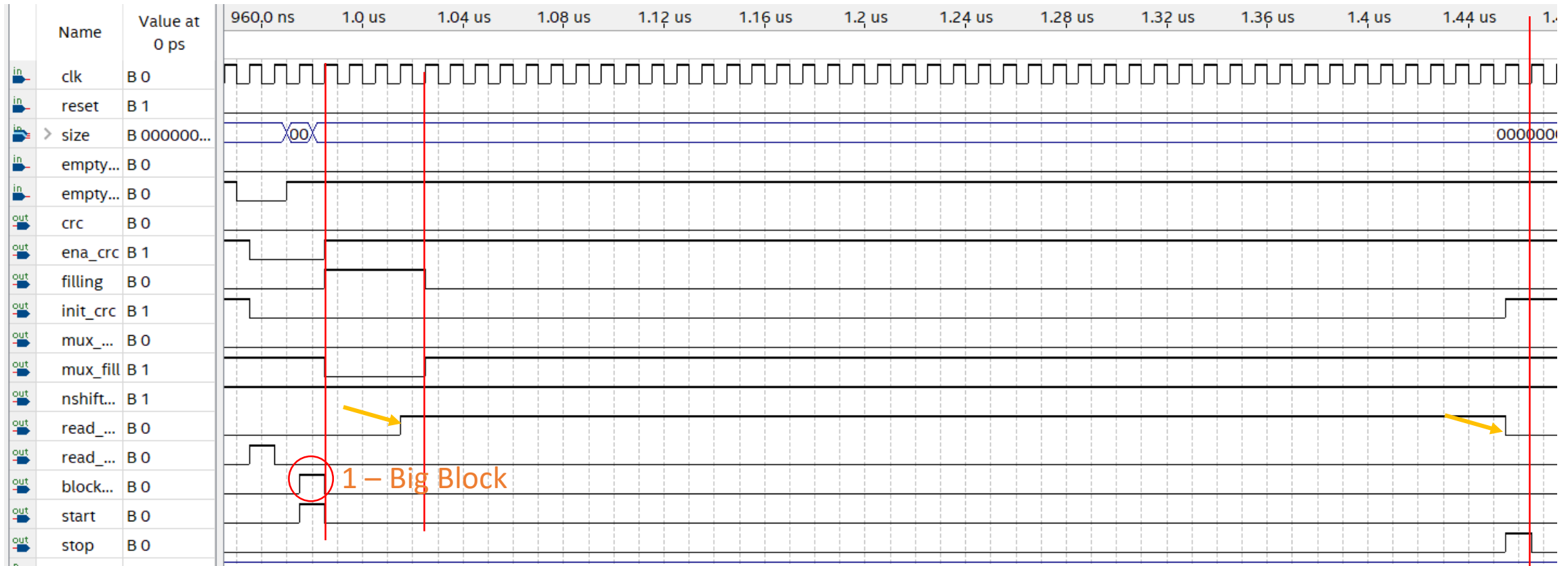


Data 44 CYCLES

- 1 big block
- 4 filler bits

Block Size Computation

- Port:
 - Input size FIFO:
 - [15:0] size_in, write request,
 - (intra-subsystem) output block size FIFO:
 - [19:0] block size & numbers , read request, empty
- The 20-bit block size data include:
 - [1:0] number of large block (6144)
 - [1:0] number of small block (1056)
 - [15:0] filler bits
 - K+ & K- removed

Block Size Computation: RTL view

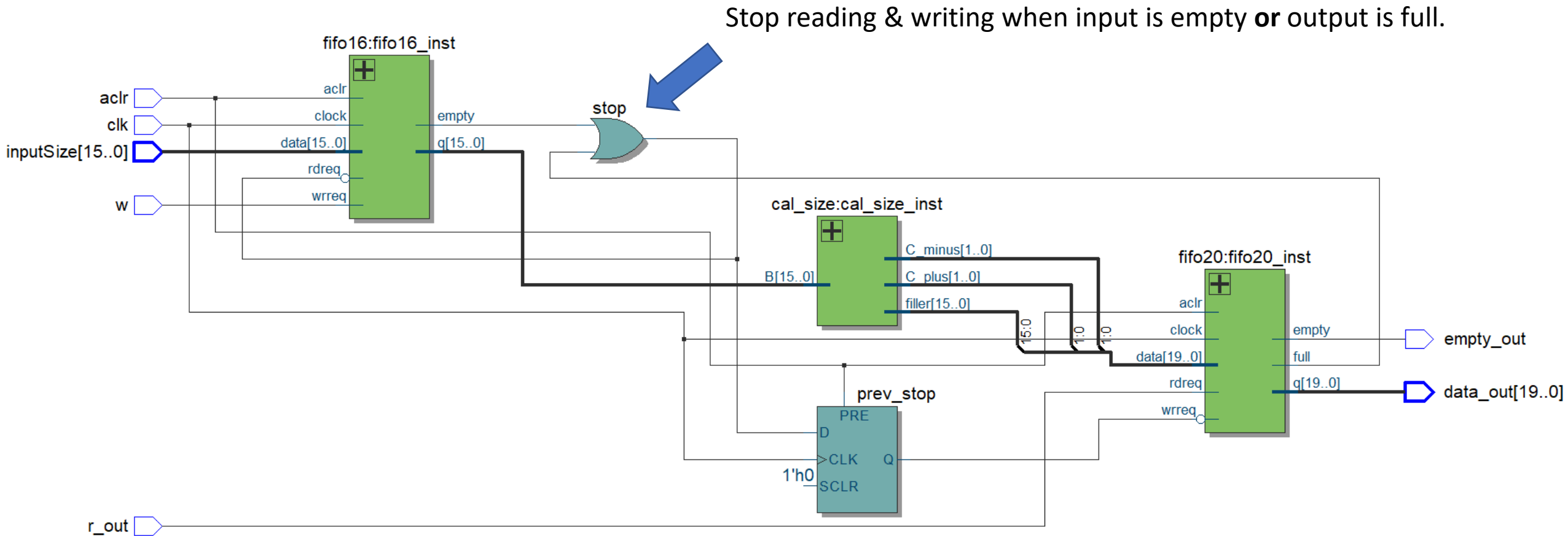


Functional Simulation

Four levels (of block size):

- 12240 (0x2fd0)
- 7152 (0x1bf0)
- 6144 (0x1800)
- 1056 (0x0420)

Writing input size

 

Read output
FIFO

Output block sizes

Block size 1
Two large blocks
Filler = 0FF0
= 2FD0 - **1FE0**

Block size 2
One large block
Filler = 0800
= 1800 - **1000**

Block size 3
One large block
One small block
Filler = 0330
= 1BF0 - **18C0**

Block size 4
One large block
Filler = 1004
= 1800 - **07FC**

Block size 4
One small block
Filler = 0401
= 0420 - **001F**

Timing & Resource Analysis


- Max Frequency
 - 111.78 MHz
- Critical Path
 - Size FIFO in size computation

Logic utilization (in ALMs)	174 / 56,480 (< 1 %)
Total registers	151
Total pins	27 / 268 (10 %)
Total virtual pins	0
Total block memory bits	5,248 / 7,024,640 (< 1 %)
Total RAM Blocks	3 / 686 (< 1 %)
Total DSP Blocks	0 / 156 (0 %)

Simulation with Modelsim

- Python script generating simulation patterns
 - Generate random input vector with given size
 - Calculate block size & filler size
 - Generate multiple segmented blocks according to those sizes
 - Calculate CRC for each block
 - Generate correct outputs (MSB -> CRC + segmented block + *filler -> LSB)
- Run modelSim through testbenches
 - Feed the input vector (one bit/cycle)
 - Print the waveform of correct outputs according to control signals
 - Compare the waveform of outputs with correct ones

Simulation with Modelsim

 

Filler flag switch to 0

Correct output vector generated from python script